

# **Lecture 3 (Chapter 2)**

## **Introduction to VHDL**


Khaza Anuarul Hoque  
ECE 4250/7250

# Introduction

- With the allowance of more and more components on a chip, digital systems have continued to grow in complexity.
- Technology improvements have advanced the very large scale integration (VLSI) field. Despite changes in integration ability, the term VLSI remains popular.
- Early integrated circuits belonged to small-scale integration (SSI), medium-scale integration (MSI), or large-scale integration (LSI) groups depending on the density of integration.

# Computer-Aided Design (CAD)


- Steps in modern digital system design:

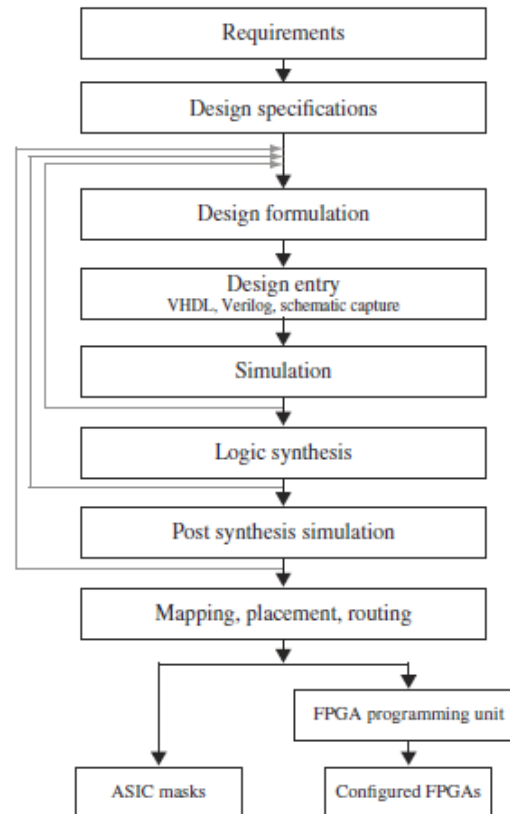

# CAD (continued)

- Target technologies that are available:

FIGURE 2-2: Spectrum of Design Technologies

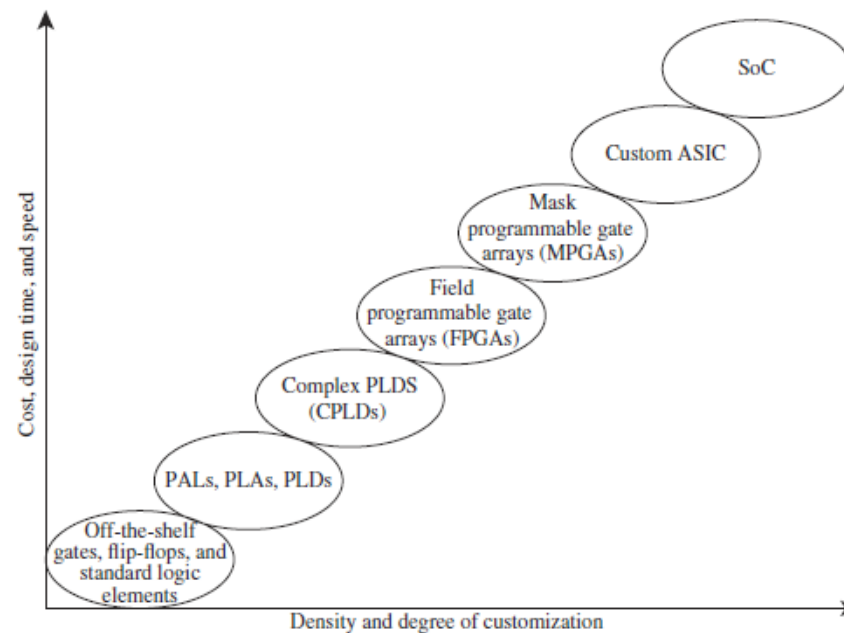

- Most common: field programmable gate arrays (FPGAs) and application-specific integrated circuits (ASICs).

# Hardware Description Languages (HDLs)

- Two popular HDLs—VHDL and Verilog.
- VHDL is an HDL used to describe the behavior and/or structure of digital systems.
- VHDL can describe a digital system at several different levels—behavioral, data flow, and structural.
- VHDL leads naturally to a top-down design methodology.


# VHDL Description of Combinational Circuits

- VHDL models combinational circuits using **concurrent** statements.
- Concurrent statements:
  - Statements that are **always ready** to execute.
  - Evaluated any time and every time a signal on the right side of the statement changes.
  - Execute repeatedly as if they were in a loop.

# VHDL Description of Combinational Circuits (continued)

- Concurrent statements (continuous assignments) example:


FIGURE 2-3: A Simple Gate Circuit

 

```
C <= A and B after 5 ns;  
E <= C or D after 5 ns;
```

```
C <= A and B;  
E <= C or D;
```

 
# VHDL Description of Combinational Circuits (continued)



```
CLK <= not CLK after 10 ns;
```



```
CLK <= not CLK;
```

 

```
-- when A changes, these concurrent  
-- statements all execute at the  
-- same time
```

```
D <= A and B after 2 ns;
```


```
E <= not A after 1 ns;
```

```
F <= A or C after 3 ns;
```


 
# VHDL Modules

- The general structure of a VHDL module is an **entity** description and an **architecture** description.
- **Entity** description declares the input and output signals.
- **Port** declaration specifies the inputs and outputs to the module.
- **Architecture** specifies the internal operation of a module.



```
entity two_gates is  
  port(A, B, D: in bit; E: out bit);  
end two_gates;  
  
architecture gates of two_gates is  
  signal C: bit;  
  begin  
    C <= A and B; -- concurrent  
    E <= C or D; -- statements  
  end gates;
```



# VHDL Modules (continued)

- **Mode** indicates the direction of information
- Use the **in**, **out**, and **inout** keywords to specify the direction of port signals.
- **Type** specifies the data type that can be communicated

# VHDL Modules (continued)

- Other modes:
  - **buffer**: similar to **inout**, can be read and written into the entity, helpful if the signal is an output.
  - **linkage**: useful when VHDL entities are connected to non-VHDL entities.