

Lecture 10 (Chapter 4)

Design Examples: Add-shift Multipliers

Khaza Anuarul Hoque
ECE 4250/7250

Introduction

- In any design:
 - State the problem.
 - Obtain clear design specifications.
 - Define basic building blocks necessary to accomplish what is specified, e.g., adders, shift registers, counters, etc.

Introduction (continued)


- Traditional design methodology:
 - **Data path:** hardware that performs the data processing.
 - For microprocessor: the arithmetic logic unit (ALU)
 - **Controller:** sends control signals to the data path and can obtain feedback in the form of status signals from the data path.
 - Many modifications can be made here.

Add-and-Shift Multiplier

- In $A \times B$, the first operand (A) is called the **multiplicand**, and the second operand (B) is called the **multiplier**.
- Binary multiplication process:
 - Multiplicand is shifted.
 - Next bit of multiplier is examined (also a shifting step).
 - If this bit is 1, the shifted multiplicand is added to the product.

Add-and-Shift Multiplier (continued)

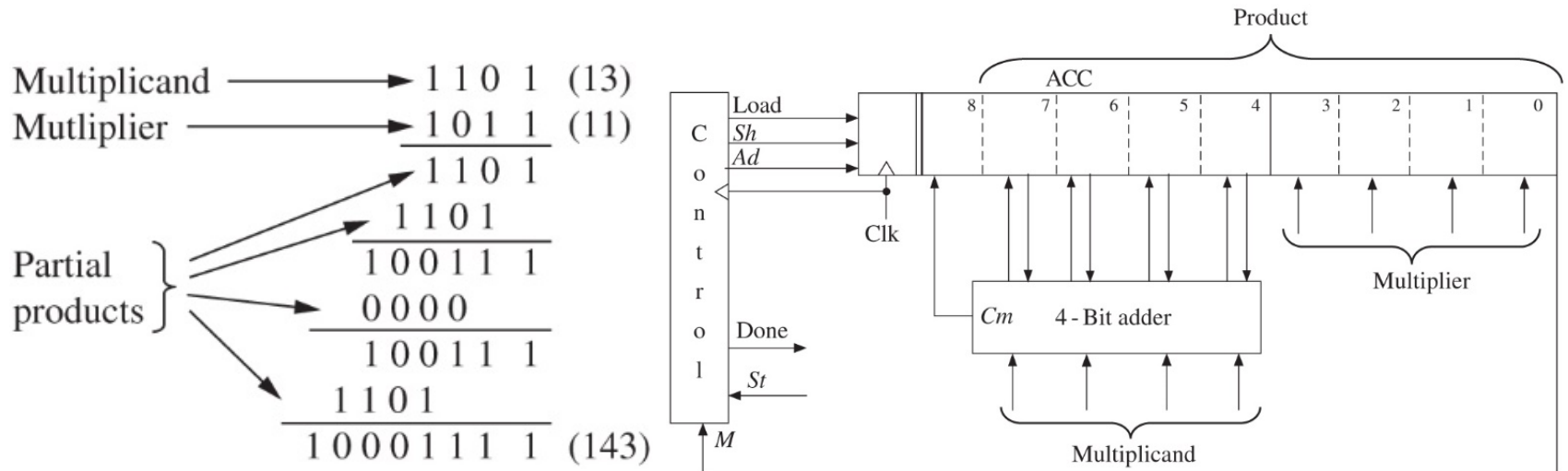- Example: multiply 13_{10} by 11_{10} in binary:



- Sometimes called a serial-parallel multiplier, as the multiplier bits are processed serially while addition takes place in parallel.

Add-and-Shift Multiplier (continued)


- Example reworked to show the location of the bits in the registers at clock time:

initial contents of product register	0 0 0 0 0 1 0 1 1	← M (11)
(add multiplicand since $M = 1$)	1 1 0 1	(13)
after addition	0 1 1 0 1 1 0 1 1	
after shift	0 0 1 1 0 1 1 0 1	← M
(add multiplicand since $M = 1$)	1 1 0 1	
after addition	1 0 0 1 1 1 1 0 1	
after shift	0 1 0 0 1 1 1 1 0	← M
(skip addition since $M = 0$)		
after shift	0 0 1 0 0 1 1 1 1	← M
(add multiplicand since $M = 1$)	1 1 0 1	
after addition	1 0 0 0 1 1 1 1 1	
after shift (final answer)	0 1 0 0 0 1 1 1 1	(143)

dividing line between product and multiplier

Add-and-Shift Multiplier (continued)

 - State graph for control circuit (designed to output the proper sequence of add and shift signals):



Behavioral model of a 4 x 4 binary ADD-Shift multiplier in VHDL


```

entity mult4X4 is
    port(Clk, St: in bit;
          Mplier, Mcand: in unsigned(3 downto 0);
          Done: out bit);
end mult4x4;

architecture behave1 of mult4x4 is
    signal State: integer range 0 to 9;
    signal ACC: unsigned(8 downto 0); -- accumulator
    alias M: bit is ACC(0);          -- M is bit 0 of ACC
begin
    process(Clk)
    begin
        if Clk'event and Clk = '1' then -- executes on rising edge of clock
            case State is
                when 0 => -- initial State
                    if St = '1' then
                        ACC(8 downto 4) <= "00000"; -- begin cycle
                        ACC(3 downto 0) <= Mplier; -- load the multiplier
                        State <= 1;
                    end if;
                when 1 | 3 | 5 | 7 => -- "add/shift" State
                    if M = '1' then -- add multiplicand
                        ACC(8 downto 4) <= '0' & ACC(7 downto 4) + Mcand;
                        State <= State + 1;
                    else
                        ACC <= '0' & ACC(8 downto 1); -- shift accumulator right
                        State <= State + 2;
                    end if;
                when 2 | 4 | 6 | 8 => -- "shift" State
                    ACC <= '0' & ACC(8 downto 1); -- right shift
                    State <= State + 1;
                when 9 => -- end of cycle
                    State <= 0;
            end case;
        end if;
    end process;
    Done <= '1' when State = 9 else '0';
end behave1;

```