

# **Lecture 12 (exercise)**


## **Array Multipliers: Problems**

Khaza Anuarul Hoque  
ECE 4250/7250

# Problem

- Using array multipliers give an **optimum** circuit for calculation of Y:
- $Y = [4 \mathbf{N} ( \mathbf{N} ) ] - 1$
- where N is a 3-bit unsigned binary number.  $N = a_2 a_1 a_0$
- Show your implementation with **N = 2**.
- Give a detailed estimate of delay and area (Full Adder, Half Adder AND gate or other entity used).
- Show the input to each adder clearly.

$$H(N) - 1 \quad N = a_2 a_1 a_0$$

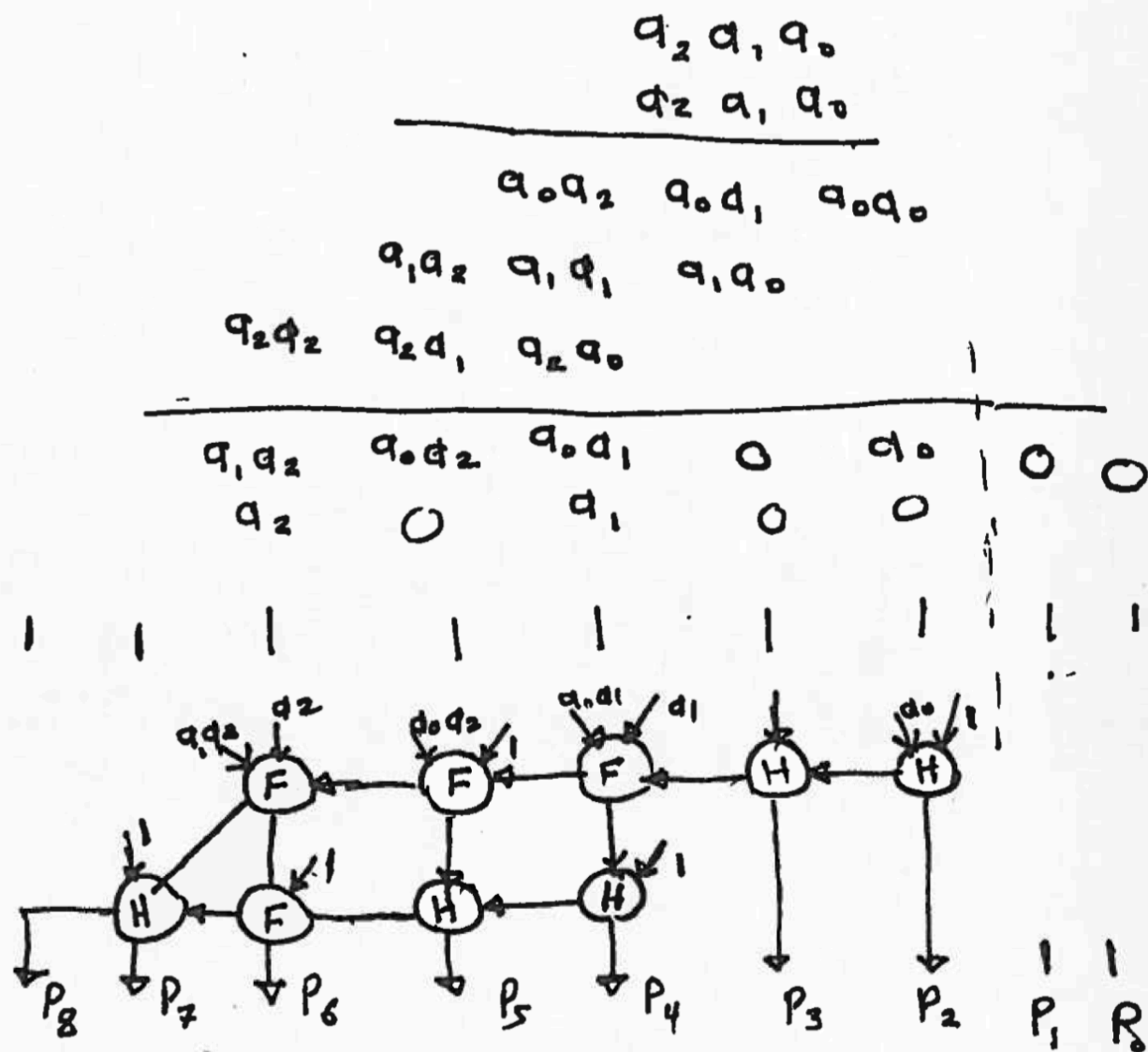

Shift 2 places to left

add -1

$$\text{Delay} = 2\gamma_H + 5\gamma_F + \gamma_{AND}$$

$$A_{\text{req}} = 4A_H + 5A_F + 9A_A$$