

Lecture 9 (Chapter 2 + more)

VHDL: Sequential design and FSM

Khaza Anuarul Hoque
ECE 4250/7250

VHDL Libraries

- Extend the functionality of VHDL.
- Define types, functions, components, and overloaded operators.
- Need a library statement and a use statement.

```
library IEEE;  
use IEEE.numeric_bit.all;
```
- The **numeric_bit** package uses bit_vectors to represent unsigned and signed binary numbers.

Modeling Registers Using VHDL


- When several flip-flops change state on the same clock edge, statements representing these flip-flops can be placed in the same clocked processes.

- Example:

```

process (CLK)
  begin
    if CLK'event and CLK = '1' then
      Q1 <= Q3 after 5 ns;
      Q2 <= Q1 after 5 ns;
      Q3 <= Q2 after 5 ns;
    end if;
  end process;

```

 

- These flip-flops all change state following the rising edge of the clock, and the three statements in the always statement execute in sequence with no delay.


Modeling Registers VHDL (cont.)

- If we were to omit the delay in the preceding example and replace the sequential statements with:

```
Q1 <= Q3;  Q2 <= Q1;  Q3 <= Q2;
```


the operation would be essentially the same. The three statements execute in sequence in zero time, and then the Q's values change after a delta delay.

Register with synchronous clear and load

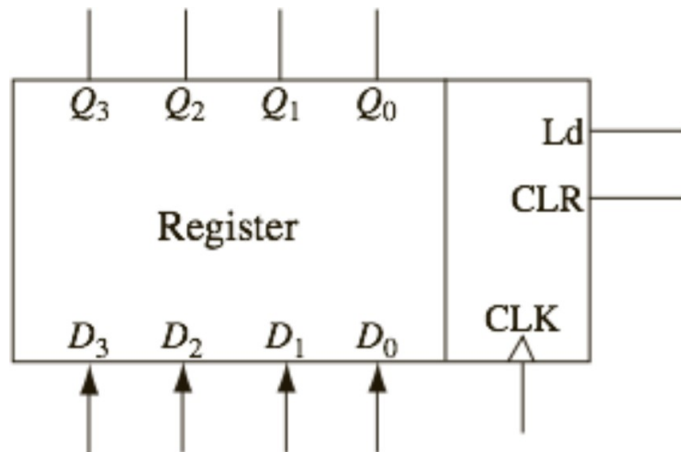

```
process(CLK)
begin
    if CLK'event and CLK = '1' then
        if CLR = '1' then Q <= "0000";
        elsif Ld = '1' then Q <= D;
        end if;
    end if;
end process;
```

 Left shift register with synchronous clear and load



```

process(CLK)
begin
  if CLK'event and CLK = '1' then
    if CLR = '1' then Q <= "0000";
    elsif Ld = '1' then Q <= D;
    elsif LS = '1' then Q <= Q(2 downto 0) & Rin;
    end if;
  end if;
end process;

```

Loops in VHDL

- Activity occurring in a repetitive way.
- Statements are sequential.
- Kinds of loop statements: **for**, **while**.
- Infinite loop:
 - General form:

```
[loop-label:] loop  
    sequential statements  
end loop [loop-label];
```
 - Can be terminated using exit statements:
exit; or **exit when** condition;

Loops in VHDL (continued)

- for loop:

- General form:

```
[loop-label:] for loop-index in range loop  
    sequential statements  
end loop [loop-label];
```

- Loop-index is incremented at the end of each loop.
 - Continues for every value in the range.

- while loop:

- General form:



```
[loop-label:] while condition loop  
    sequential statements  
end loop [loop-label];
```

- Condition is tested at the beginning of each loop.
 - Loop is terminated if condition is false.


Finite State Machines (FSMs)

- A Circuit/System/Machine that
 - Goes through a fixed number of states
 - Has fixed number of Input/Output combinations
- Used typically to
 - Control
 - Monitor
 - Calculate
 - Communication protocols, where data may be sent asynchronously or different data required different responses
 - Control of simple machine
 - Implementing simple user interfaces


FSM diagrams

  



FSM diagrams (cont.)

 

FSM diagrams fundamentals

 


FSM diagrams fundamentals

  

FSMs in VHDL

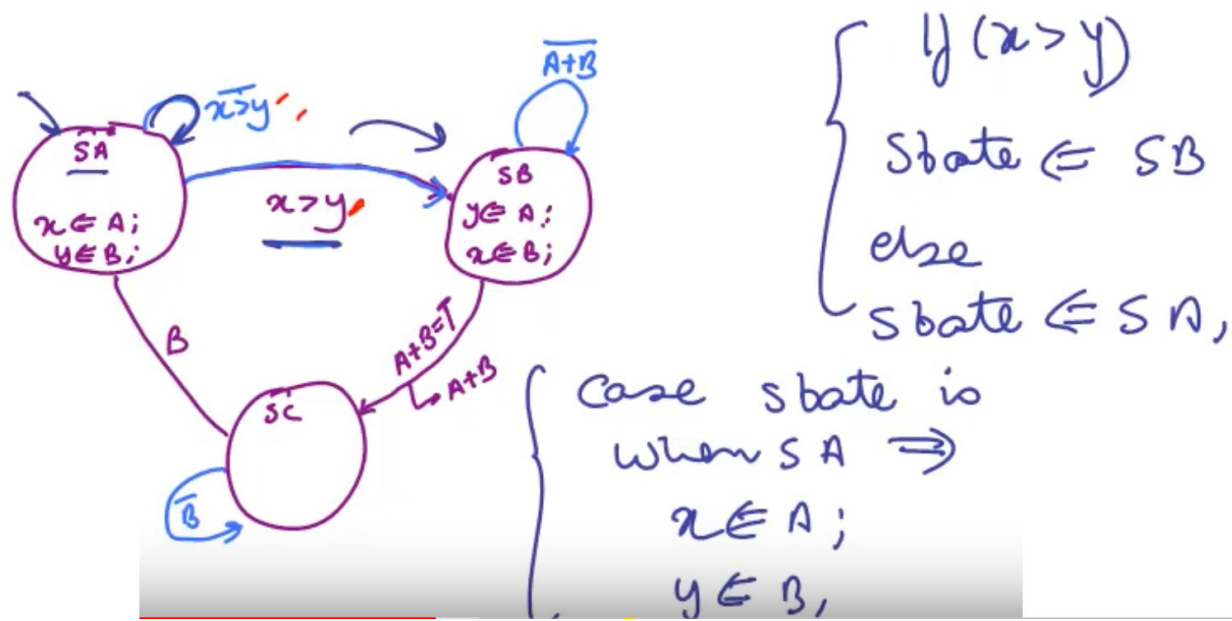- NSL is modeled using if-else statements
- Each state is modeled using Case-statements
- State variables are defined using constants
- OFL is modeled using conditional assignments



One-hot Encoding

State Variables				
State	One-Hot Code	Binary Code	Gray Code	
S0	00001	000	000	
S1	00010	001	001	
S2	00100	010	011	
S3	01000	011	010	
S4	10000	100	110	

Table 1:An example of state Encoding for a 4 state Machine

FSMs in VHDL

```

architecture Behavioral of f is

    signal x: std_logic;
    signal y: std_logic;

    constant SA : std_logic_vector(2 downto 0) := "001";
    constant SB : std_logic_vector(2 downto 0) := "010";
    constant SC : std_logic_vector(2 downto 0) := "100";
    signal state: std_logic_vector(2 downto 0) := "001";
begin
    process (clk )
    begin
        if rising_edge(clk) then

            case state is

                when SA =>

                    x <= A;
                    y <= B;


                    if ( x <= y) then -- NSL

                        state <= SA;

                    else

                        state <= SB;
                    end if; -- end of NSL
            end case;
        end if;
    end process;
end architecture;

```

 

FSMs in VHDL

```

→ when SB =>

    y <= A;
    x <= B ;

    if ( (A or B) = '1' ) then

        state <= SC;

    else
        state <= SB;
    end if;

    when SC =>

        if ( B = '1' ) then

            state <= SA;

        else
            state <= SC;
        end if;


    end case;
end if;

```

Case
 when SA
 if ! NSC
 OK
 when SB

when others =>
 state <= SA;
 good & safe design

Divider example

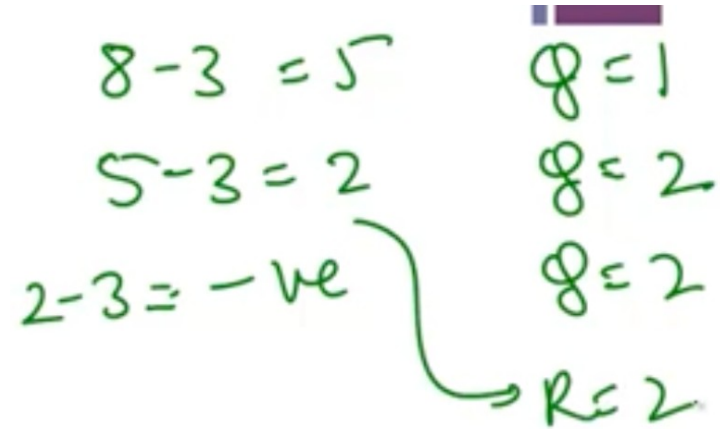


Handwritten notes illustrating a division process:

$8 - 3 = 5$	$Q = 1$
$5 - 3 = 2$	$Q = 2$
$2 - 3 = -ve$	$Q = 2$
	$R = 2$

A bracket connects the result $2 - 3 = -ve$ to the final remainder $R = 2$.

Divider example

 

Divider example

```

47 architecture Behavioral of Divider is
48
49     signal x: std_logic_vector(2 downto 0) := "000";
50     signal y: std_logic_vector(2 downto 0) := "000";
51     signal q: std_logic_vector(6 downto 0) := "0000000";
52
53
54     constant initial : std_logic_vector(2 downto 0) :=
55     constant compute : std_logic_vector(2 downto 0) :=
56     constant done : std_logic_vector(2 downto 0) := "100";
57     signal state: std_logic_vector(2 downto 0) := "001";
58
59
60 process (clk)
61
62     begin
63
64         if rising_edge(clk) then
65
66             case state is
67
68                 when initial =>
69
70                     x <= A;
71                     y <= B;
72
73                     if start = '1' then

```

```

47 architecture Behavioral of Divider is
48
49     :: std_logic_vector(2 downto 0) := "000";
50     y: std_logic_vector(2 downto 0) := "000";
51     q: std_logic_vector(6 downto 0) := "0000000";
52
53
54     at initial : std_logic_vector(2 downto 0) := "001";
55     at compute : std_logic_vector(2 downto 0) := "010";
56     at done : std_logic_vector(2 downto 0) := "100";
57     state: std_logic_vector(2 downto 0) := "001";
58
59
60 process (clk)
61
62
63
64     if rising_edge(clk) then
65
66         case state is
67
68             when initial =>
69
70                 x <= A;
71                 y <= B;
72
73                 if start = '1' then

```

Divider example

```

58 begin
59
60 process (clk)
61
62     begin
63
64         if rising_edge(clk) then
65
66             case state is
67
68                 when initial =>
69
70                     x <= A;
71                     y <= B;
72
73                     if start = '1' then
74                         state<= compute;
75                     else
76                         state<= initial;
77                     end if;
78
79                 when compute =>

```

```

59
60 process (clk)
61
62     begin
63
64         if rising_edge(clk) then
65
66             case state is
67
68                 when initial =>
69
70                     x <= A;
71                     y <= B;
72
73                     if start = '1' then
74                         state<= compute;
75                     else
76                         state<= initial;
77                     end if;
78
79                 when compute =>
80
81
82
83                     if x >= y then
84                         x <= x-y;
85                         q <= q+1;

```

Divider example

```

86
87
88
89
90
91
92
93
94
95
96
97
98
99
100
101
102
103
104
105
106
107
108
109
110

    end if;

    if x >= y then
        state<= compute;
    else
        state <= done;
    end if;

when done =>

    R <= x;
    state <= initial;

when others =>

    state <= initial;

end case;
end if;
end process;

```

```

89
90
91
92
93
94
95
96
97
98
99
100
101
102
103
104
105
106
107
108
109
110
111
112
113
114

    if x >= y then
        state<= compute;
    else
        state <= done;
    end if;

when done =>

    R <= x;
    state <= initial;

when others =>

    state <= initial;

end case;
end if;
end process;

end Behavioral;

```